



# Microprocessors

COE 381

WEEK 2: BASIC COMPUTER ORGANIZATION






# Microprocessors & Microcontrollers





# Basic Computer Organization

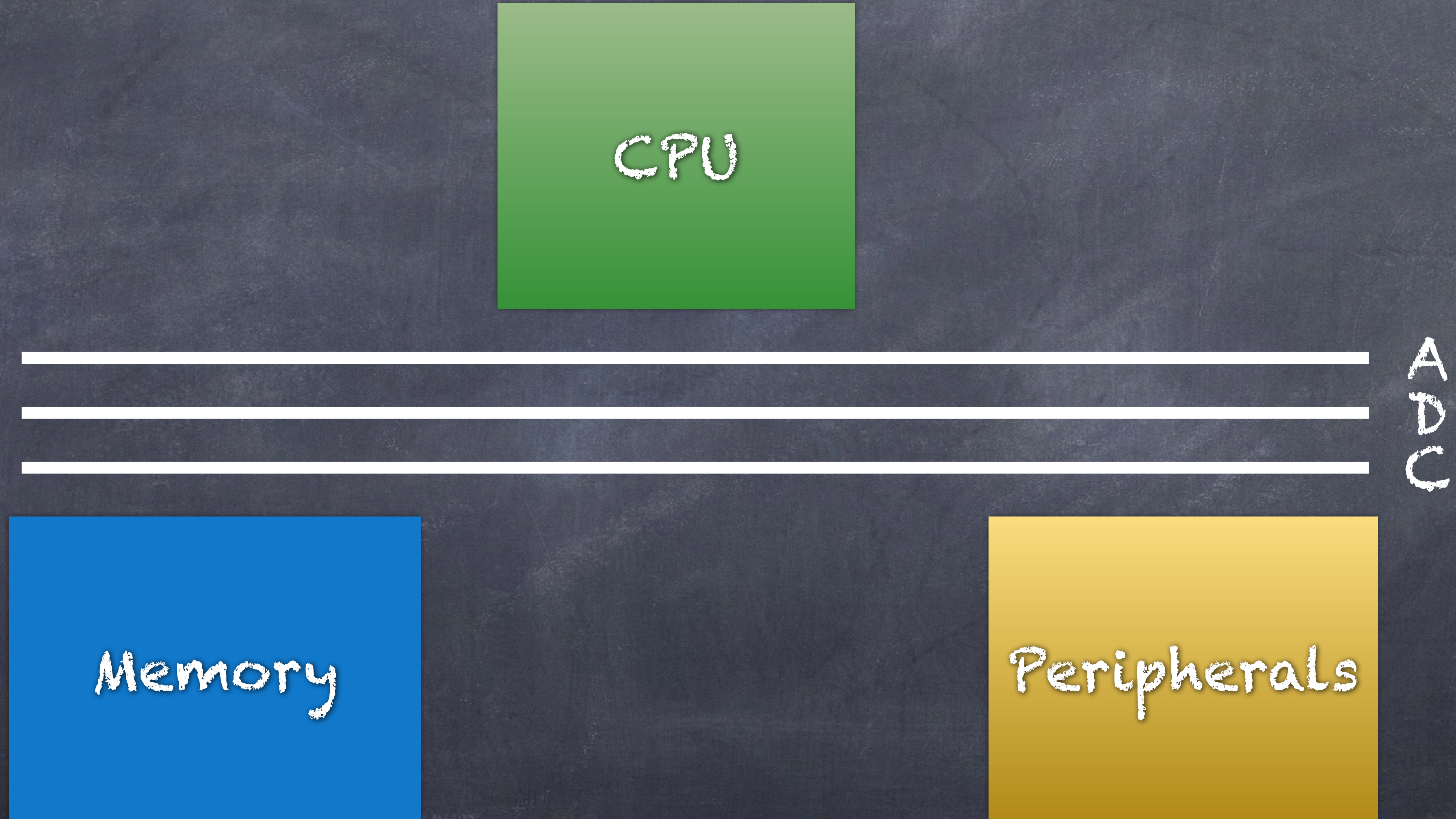





# Memory Interfacing Problem

Example:

Consider a CPU with a 16 bit address bus and an 8-bit data bus.

How do you interface 8 memory chips (2K x 4 bit) with it?





# Memory







# Memory

Address  
Bus



CS



Data  
Bus



Read  
 $\overline{RD}$

Write  
 $\overline{WR}$





# Memory Interfacing: ROM & RAM

Example:

8KB ROM, 16KB RAM.

CPU  $\Rightarrow$  16 bit Address Bus, 8 bit Address Bus.

ROM Starting Address = 0000H

RAM Starting Address = 8000H

ROM/RAM Size = 4KB





# Reading Assignment

- <https://www.youtube.com/watch?v=nL34zDTPKcs>
- Arduino Architecture – <http://meseec.ce.rit.edu/551-projects/fall2017/2-3.pdf>
- Arduino Uno Datasheet – <https://docs.arduino.cc/resources/datasheets/A0000066-datasheet.pdf>
- Docs – <https://docs.arduino.cc>